

# THE 741 OPERATIONAL AMPLIFIER

V.Ryan © 2000 - 2009

On behalf of The World Association of Technology Teachers

## W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website ([www.technologystudent.com](http://www.technologystudent.com)) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.  
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.  
NOT FOR COMMERCIAL USE.  
THIS WORK IS PROTECTED BY COPYRIGHT LAW.  
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN [www.technologystudent.com](http://www.technologystudent.com)

# THE 741 OPERATIONAL AMPLIFIER

V.Ryan © 2009 World Association of Technology Teachers

1. The 741 Operational Amplifier has two inputs. Name each one.

INPUT : \_\_\_\_\_

INPUT : \_\_\_\_\_


2. What is the main function of the operational amplifier?

\_\_\_\_\_  
\_\_\_\_\_

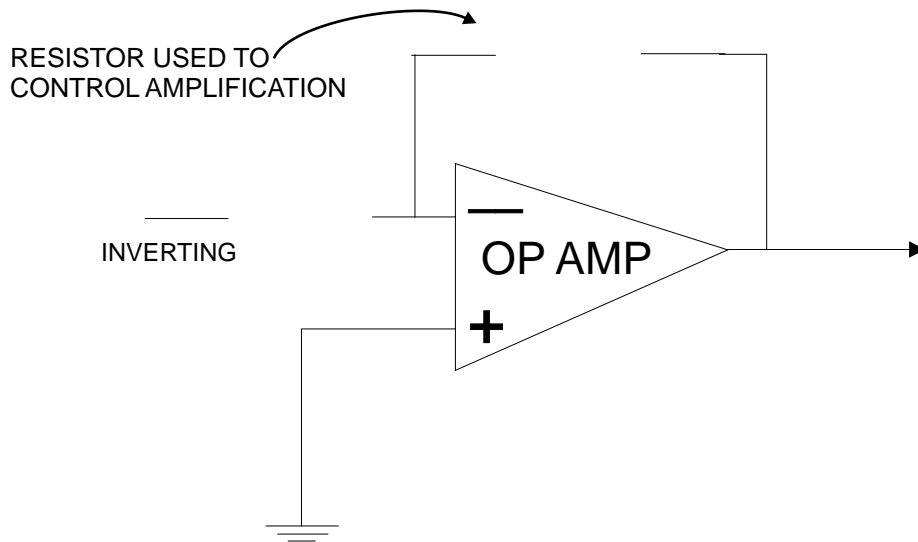3. Complete the diagram of the inverting amplifier / Op Amp shown below.


Label the inputs, output, voltage in and voltage out - using the correct names/letters.

Add the missing resistors and label each one.




4. The two main types of 741 operational amplifier are seen below. Underneath each Op Amp diagram, explain what happens to the polarity of the input signal.

INVERTING AMPLIFIER

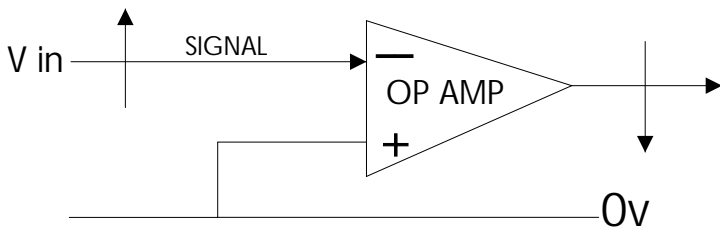

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

NON INVERTING AMPLIFIER

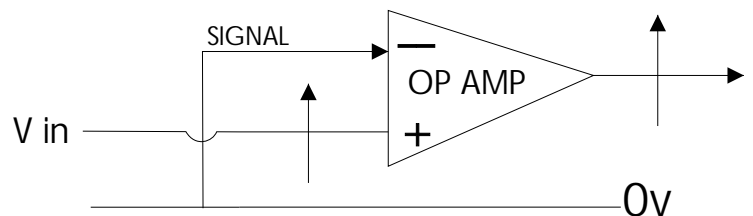

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_