

TRICOLOUR LIGHT EMITTING DIODES (LEDs) - EXAMINATION QUESTIONS

HELPFUL LINK: https://technologystudent.com/elec_flsh/tricolour1.html

1. What is a tricolour LED? Include a diagram of a tricolour LED to support your answer. **3 marks**

NOTES:

DIAGRAM

2. Explain / describe, what is being shown by both the circuits shown below. **4 marks**

