

# THE GENIE E18 PROJECT BOARD

V.Ryan © 2000 - 2010

On behalf of The World Association of Technology Teachers

## W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website ([www.technologystudent.com](http://www.technologystudent.com)) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.  
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.  
NOT FOR COMMERCIAL USE.  
THIS WORK IS PROTECTED BY COPYRIGHT LAW.  
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN [www.technologystudent.com](http://www.technologystudent.com)

# THE GENIE E18 PROJECT BOARD

V.Ryan © 2010 World Association of Technology Teachers

1. The main components of the GENIE E18 project board/ microcontroller circuit, are named below. On the 3D drawing, write each name alongside its position on the circuit board.

RESET SWITCH

BATTERY  
PACK

DRIVER  
INTEGRATED CIRCUIT


FIVE INPUTS

EIGHT OUTPUTS

GENIE E18 PIC  
MICROCONTROLLER

DOWNLOAD  
SOCKET

STATUS LED

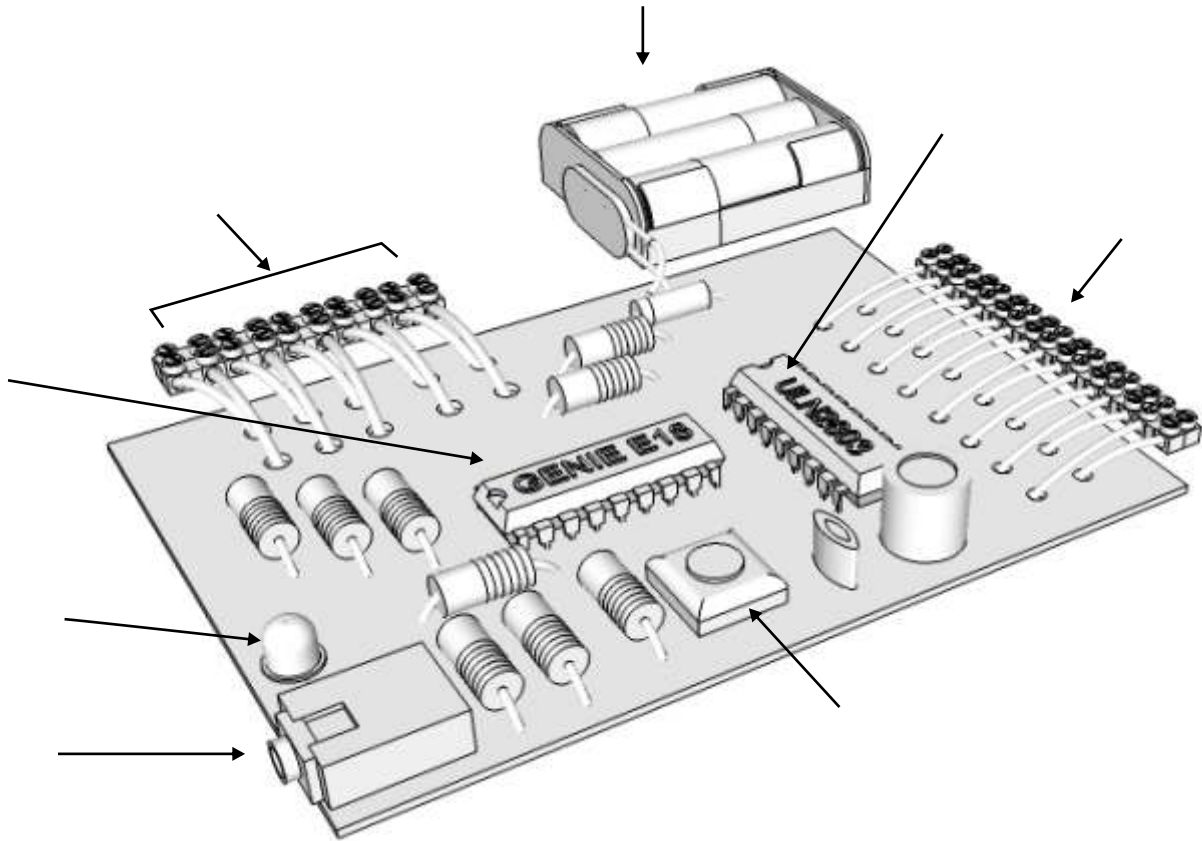

2. Why is a ULN2003 driver IC an important component in the microcontroller circuit, drawn above?

---



---



---

3. The microcontroller circuit shown above, has a number of outputs. How many outputs?

---

4. A number of components are listed below. Tick alongside all those that are outputs and cross alongside those that are inputs.

SOLENOID

MOTOR

REED SWITCH

BULB

TOGGLE SWITCH

LED

PUSH SWITCH

PIEZO BUZZER

SLIDE SWITCH

LDR LIGHT DEPENDENT RESISTOR