

# POTENTIOMETERS / VARIABLE RESISTORS

V.Ryan © 2000 - 2010

On behalf of The World Association of Technology Teachers

## W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website ([www.technologystudent.com](http://www.technologystudent.com)) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.  
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.  
NOT FOR COMMERCIAL USE.  
THIS WORK IS PROTECTED BY COPYRIGHT LAW.  
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN [www.technologystudent.com](http://www.technologystudent.com)

# POTENTIOMETERS / VARIABLE RESISTORS


V.Ryan © 2010 World Association of Technology Teachers



POTENTIOMETER

 1. A typical potentiometer / variable resistor is drawn on the left.

On the right, draw the electronic symbol that represents this important component.



SYMBOL

2. Why are potentiometers / variable resistors used in temperature sensing circuits?

---




---



---

3. What is the range of resistance of a 100k potentiometer / variable resistor?

---

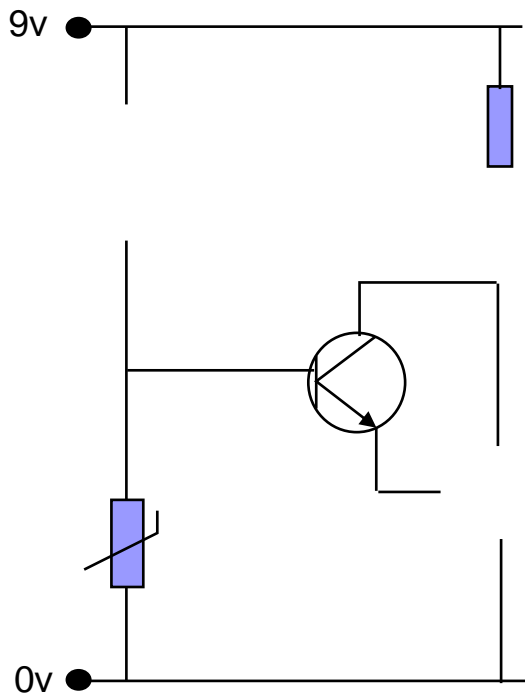

4. An incomplete temperature sensing circuit is seen opposite. The components are named below.

Complete the circuit diagram.

Write the correct component name alongside each symbol, in the circuit.

LED

PRESET  
RESISTOR

TRANSISTORS

THERMISTOR

5. Describe how the temperature sensing circuit (seen above) works. Explain the role of the potentiometer / variable resistor.

---



---



---



---

6. How are potentiometers / variable resistors very similar to preset resistors?

---



---