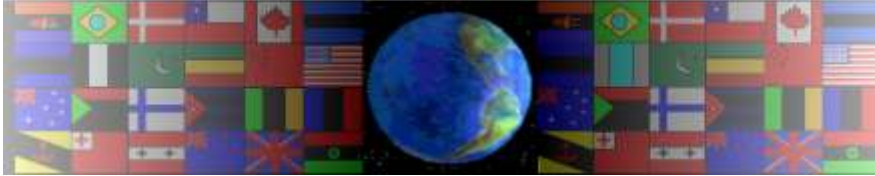


THE 555 IC

V.Ryan © 2000 - 2009

On behalf of The World Association of Technology Teachers

W.A.T.T.



World Association of Technology Teachers


This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.
NOT FOR COMMERCIAL USE.
THIS WORK IS PROTECTED BY COPYRIGHT LAW.
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN www.technologystudent.com

EXAMINATION QUESTION


V.Ryan © 2009 World Association of Technology Teachers

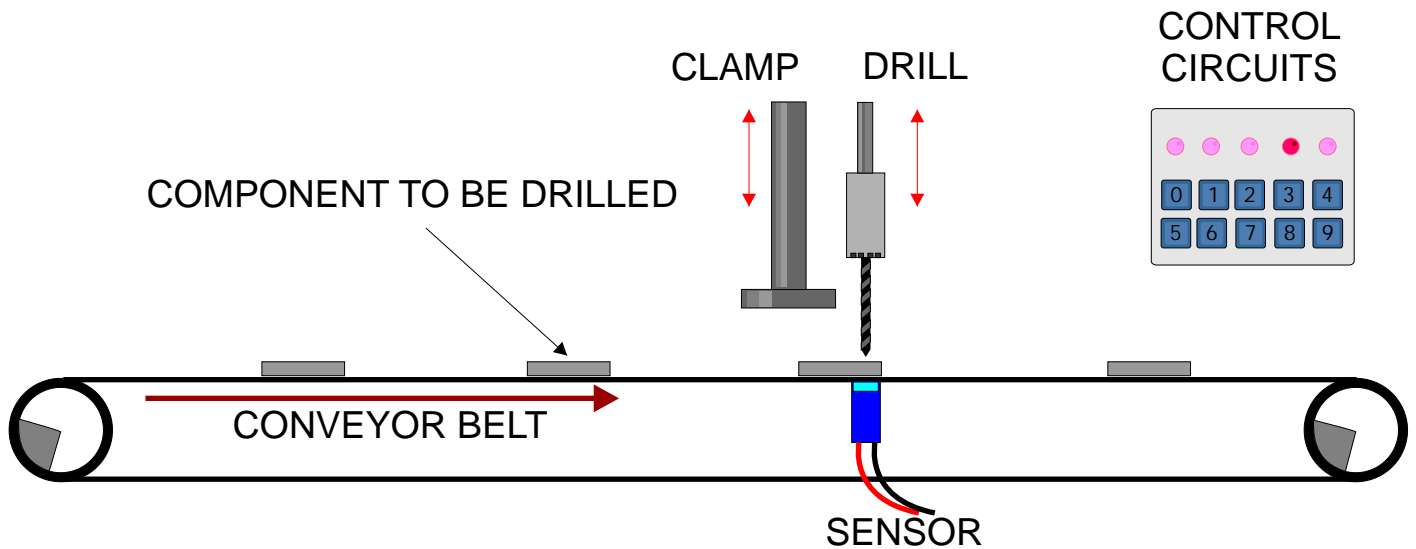1. The following question is based on the 555 monostable circuit. The circuit shown is part of a production line and controls the timing sequence. The automated production line is shown below. Parts / components move along the production line where they are sensed, clamped down, drilled and then released, moving down the production line again. The 555 monostable circuit controls the timing of the entire production line.



The timer circuit is found inside the control circuit box. The incomplete circuit diagram is found below. Add the following components to complete the timer circuit:

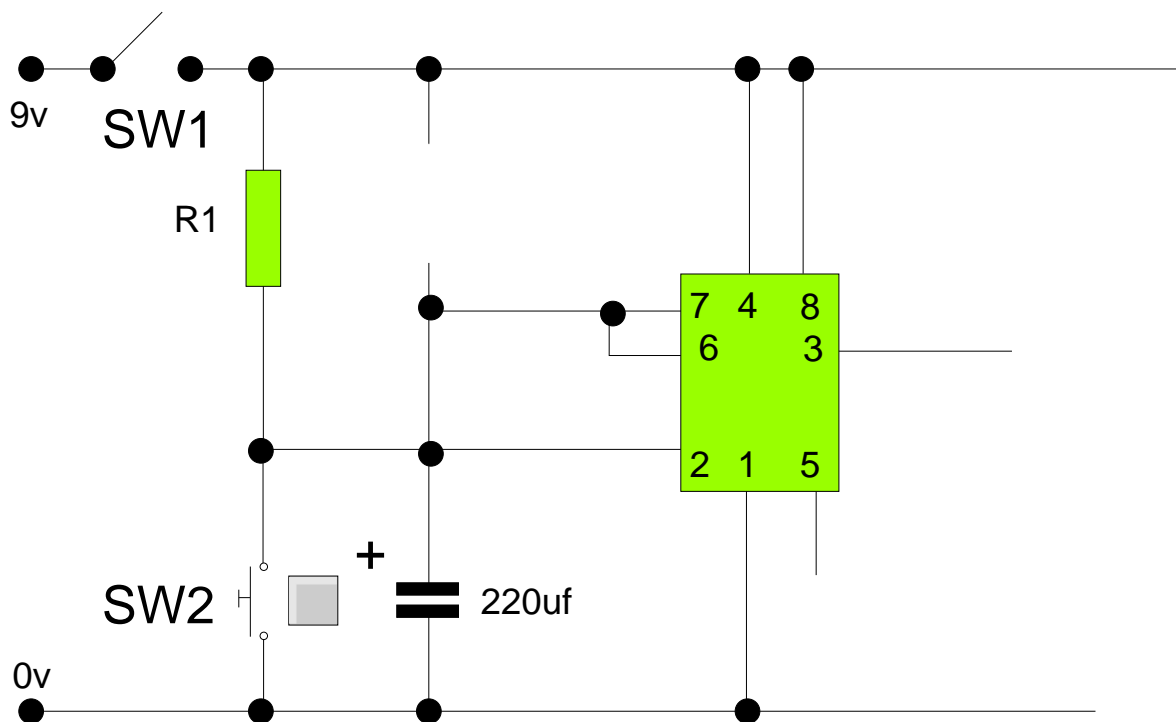- A. 0v and 9v supply
- B. A variable resistor for altering the length timing sequence.
- C. A buzzer that sounds during the timing sequence.



D. Explain how your completed circuit works.

2. What is the role of the variable resistor and capacitor?


3. The 555 timer is an IC. What does IC mean?

4. The 555 timer has a DIL layout. What does DIL mean?

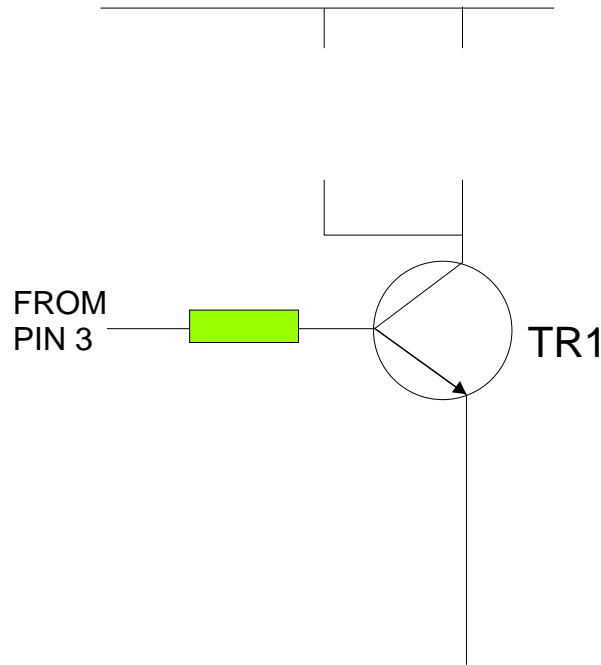5. It has been found that the sound emitted by the buzzer is too low. A circuit designer has suggested that a relay be added. The circuit also needs protecting by the addition of another component placed in parallel with the relay. (See layout below)

Complete the circuit diagram by adding the relay and a suitable additional 'protecting' component.

V.Ryan © 2009 World Association of Technology Teachers



6. Name the component that protects the circuit and explain how it does this.

NAME: _____

How the component protects the circuit.

7. What is back EMF ?
