
## **DARLINGTON PAIR - BREADBOARD**

V.Ryan © 2000 - 2009

On behalf of The World Association of Technology Teachers

W.A.T.T.

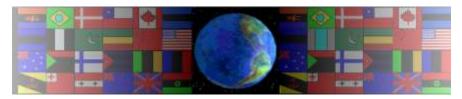

World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet.

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.

THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.


NOT FOR COMMERCIAL USE.

THIS WORK IS PROTECTED BY COPYRIGHT LAW.

IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN www.technologystudent.com
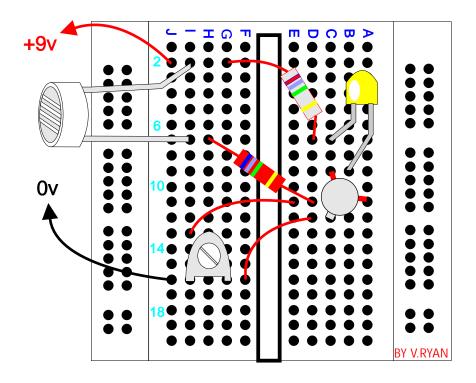
# BREADBOARD PROJECT

V.Ryan © 2009 World Association of Technology Teachers



## Components:


680 ohm resistor to protect the LED.

1K resistor from LDR to the base of the NPN transistor.

One BFY50 npn transistor (try any alternative).

One 10K preset resistor. One LDR.

### TRANSISTOR LAYOUT

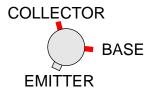

1. Build the breadboard circuit shown above. This is a dark sensor and relies on several components, in particular the transistor. When the LDR is covered the LED will light, although there may be a need to alter the setting of the preset resistor.

#### How it works:

When light shines into the LDR its resistance is high and consequently current cannot flow from positive 9 volts to negative 0 volts. If the LDR is completely covered its resistance falls dramatically. Current then flows into the base of the transistor switching it on. Consequently current can flow through the collector and emitter - therefore, the LED lights.

- 2. Try building a light sensor, that is a circuit in which the LED lights if light shines into the LDR. HINT; try swapping round the LDR and the preset resistor.
- 3. Try building a similar circuit but this time add an arrangement of transistors called a Darlington Pair. Do you find any difference in the operation of the circuit?
- 4. Try building a similar dark sensor but this time with a relay rather than an LED.