

555 TIMER AND CAM EXAMINATION QUESTIONS

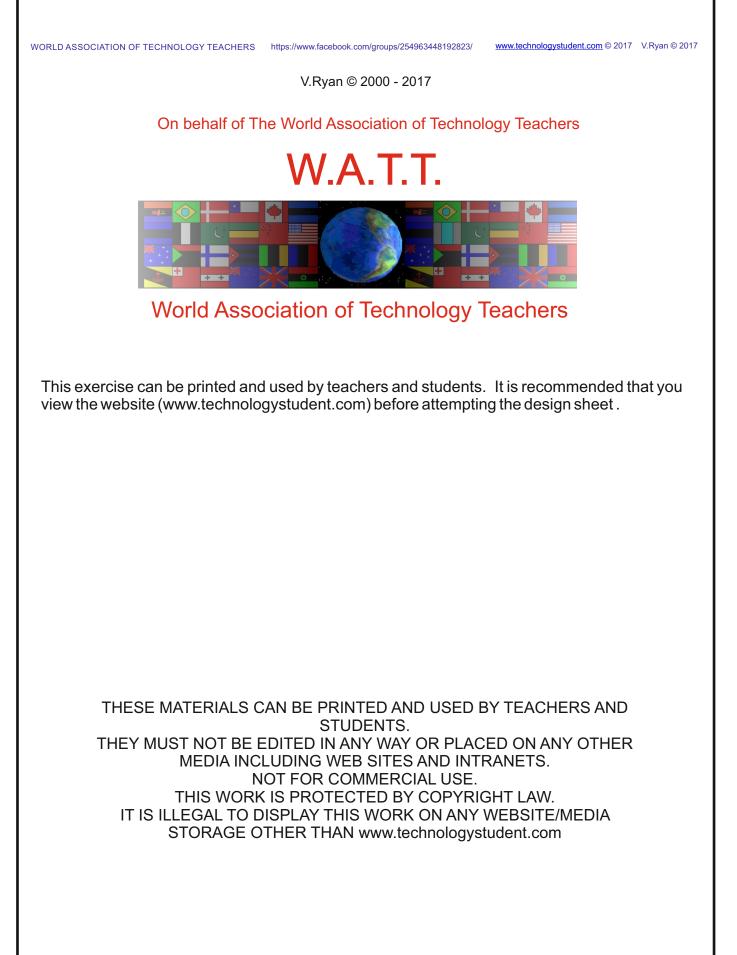


555 TIMER AND CAM EXAMINATION QUESTIONS

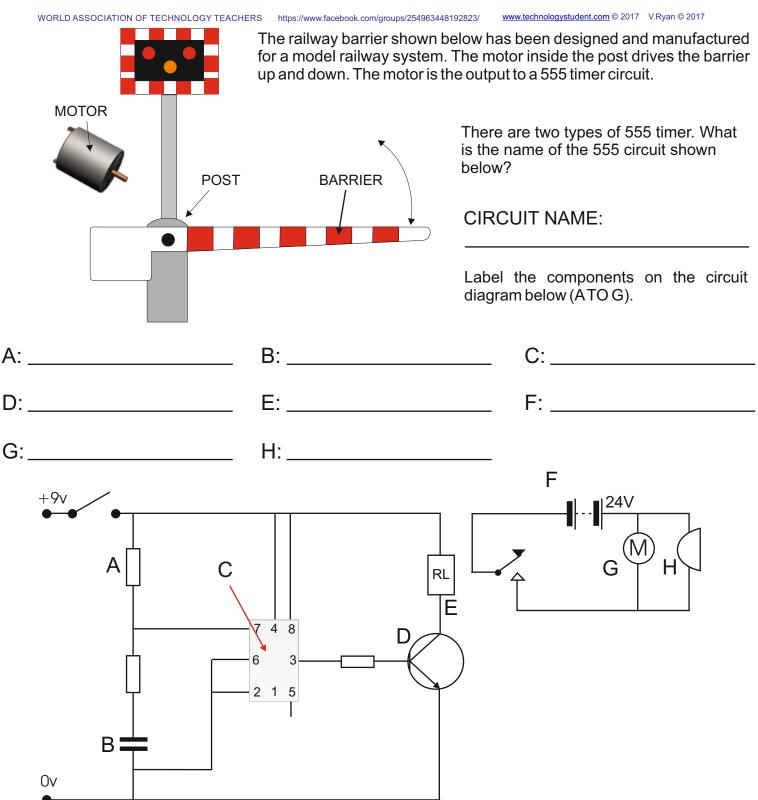

The relay is causing major problems because an important component is missing. Name the component and draw its symbol in the correct position on the circuit diagram above.

COMPONENT NAME:

What is the function of the component ?

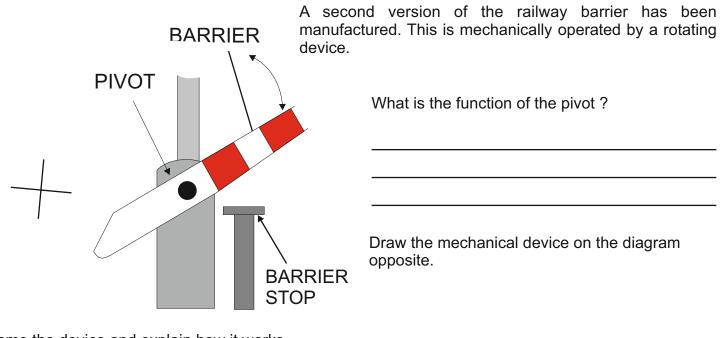

Name the device and explain how it works.

NAME:

HOW IT WORKS:

What is the function of the barrier stop ?