

THE PICAXE-08 MICROCONTROLLER PROJECT BOARD

V.Ryan © 2000 - 2010

On behalf of The World Association of Technology Teachers

W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.
NOT FOR COMMERCIAL USE.
THIS WORK IS PROTECTED BY COPYRIGHT LAW.
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN www.technologystudent.com

THE PICAXE-08 MICROCONTROLLER PROJECT BOARD

V.Ryan © 2010 World Association of Technology Teachers

1. The diagram below, shows a PICAXE 08 starter kit.


Write an overall description/explanation which includes the following:


A general description of a PICAXE 08 Starter Kit.

How it is connected to the computer.

Power source.

Jumper Switch.

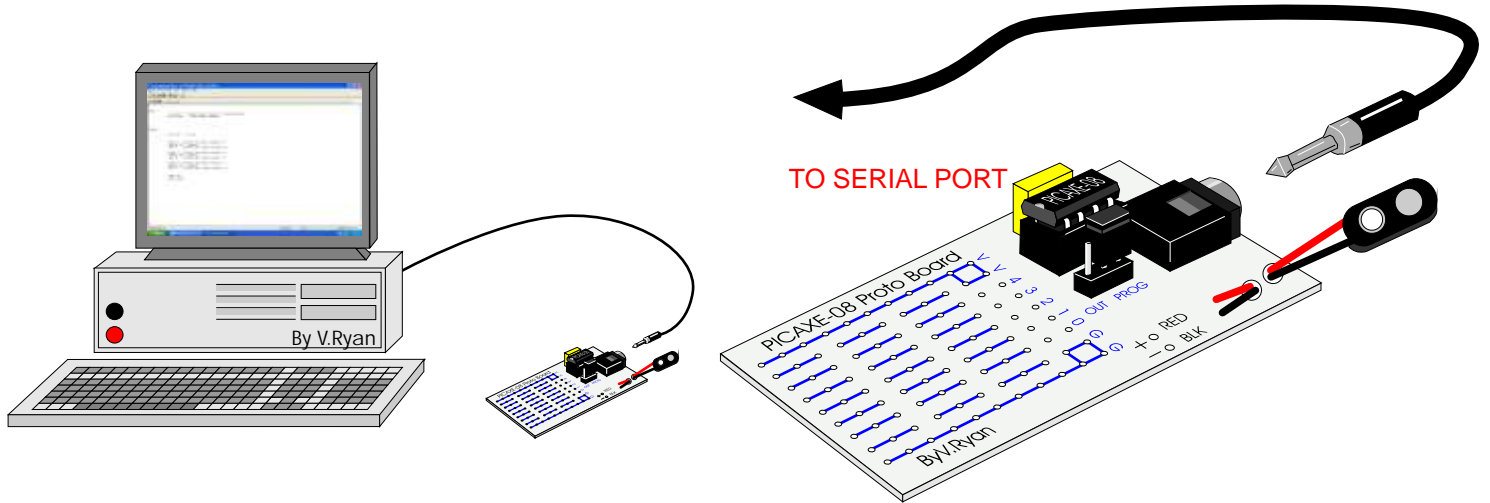

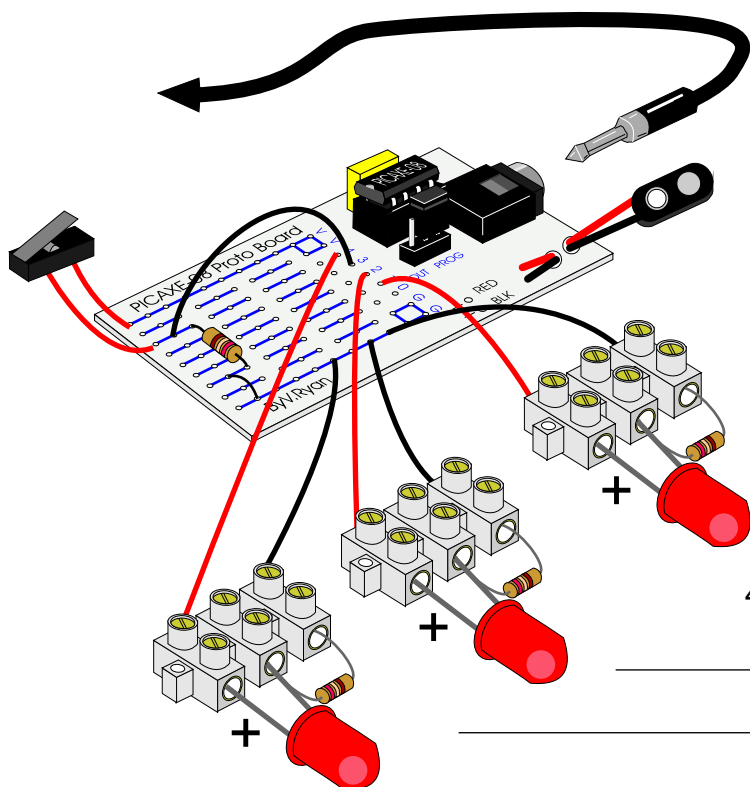

2. What type of switch is connected to pin 3?

3. What components protect the LEDs?

4. The starter board has a 3 to 5 volt power supply. Why do the LEDs need protecting?

4. How could you use this circuit, in a practical situation?
