

V.Ryan © 2010 World Association of Technology Teachers

## **INDIVIDUAL RESEARCH**



V.Ryan © 2010 World Association of Technology Teachers I am researching a range of electronic components and circuits that could be useful for my security device project.

## INDIVIDUAL RESEARCH PRODUCT: SECURITY DEVICE ELECTRONICS - INPUTS - PROCESSING AND OUTPUTS

Most security devices depend on a PIC Microcontroller, programmable circuit. This type of circuit could be used in my project, as PICs can be reprogrammed any number of times. Basic PIC Microcontrollers are relatively cheap and reliable. I intend to programme my PIC Microcontroller so that an INPUT such as a light sensor or pressure pad or micro-switch will detect movement and then activate security shutters and an alarm, plus flashing lights.



I will use a computer and software to programme the microcontroller. I will simulate the programme on screen so that obvious faults can be corrected.

When I am happy with the programme, I will download it to my PICAXE circuit, ready for use.

I will consider using LEDs, motors and sound outputs with my circuit / security device.



The PICAXE-08 Starter Pack may be suitable for my project as it has a limited number of inputs/outputs. The pack includes a PCB and all the components needed to manufacture a programmable circuit with 5 inputs/outputs.

## PLAN / BIRDS EYE VIEW OF A PICAXE-08 PROJECT BOARD



The circuit above shows how both input and output devices can be connected to the PICAXE-08.

The example circuit is for my security device. When an intruder stands on the pressure pad close to the front door, the PICAXE microcontroller detects an input. The programme within the microcontroller then outputs at pin 6, energising a relay. This allows a second circuit to turn on a motor, that closes security shutters at the windows and doors.