LIGHT/DARK SENSOR, DARLINGTON PAIR, DIODE AND RELAY


WORLD ASSOCIATION OF TECHNOLOGY TEACHERS https://www.facebook.com/groups/254963448192823/

www.technologystudent.com © 2017 V.Ryan © 2017

V.Ryan © 2000 - 2017

On behalf of The World Association of Technology Teachers

W.A.T.T.

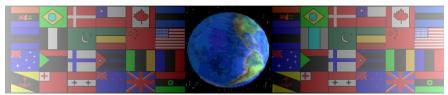


World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet.


THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS. THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS. NOT FOR COMMERCIAL USE. THIS WORK IS PROTECTED BY COPYRIGHT LAW. IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN www.technologystudent.com

LIGHT/DARK SENSOR, DARLINGTON PAIR, DIODE AND RELAY

As part of a GCSE project a student has designed a barrier system for a roller coaster platform. The specification drawn up by the student says - As a carriage approaches the platform it breaks a light beam and the barrier is lowered, stopping excited and unruly riders getting too close to the stopping carriages. When the full carriage moves away, the barrier should lift allowing the next set of riders to access the platform, ready for the next carriage.

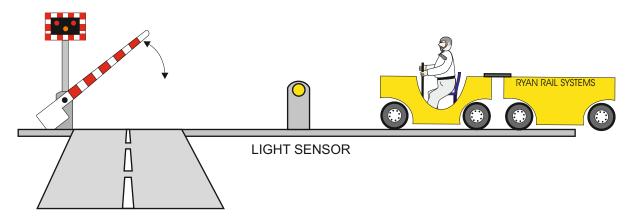

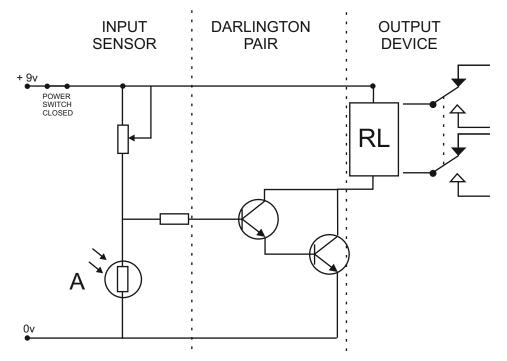The student's prototype control circuit can be seen below.



Name component 'A'.


Give one reason why the circuit shown above will not meet the specification.

Write a modification that would solve the problem with the specification

Why is a darlington pair positioned between the sensor and the relay?

The darlington pair circuit has been tested but it regularly fails. Draw a modification on the circuit diagram below that will ensure that the circuit works without problems.

V.Ryan © 2008

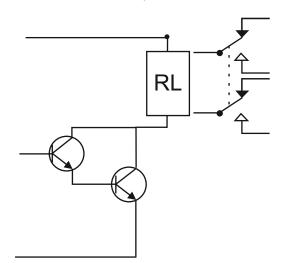

Explain how your modification works.