## SYSTEMS DIAGRAM AND TEMPERATURE SENSOR

WORLD ASSOCIATION OF TECHNOLOGY TEACHERS


https://www.facebook.com/groups/254963448192823/

www.technologystudent.com © 2017 V.Ryan © 2017

V.Ryan © 2000 - 2017

On behalf of The World Association of Technology Teachers

W.A.T.T.

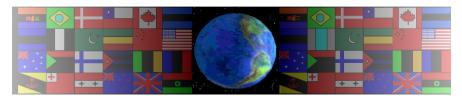

## World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet.

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.

THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.

NOT FOR COMMERCIAL USE.

THIS WORK IS PROTECTED BY COPYRIGHT LAW.

IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA

STORAGE OTHER THAN www.technologystudent.com

## SYSTEMS DIAGRAM AND TEMPERATURE SENSOR

WORLD ASSOCIATION OF TECHNOLOGY TEACHERS https://www.facebook.com/groups/254963448192823/


A roller coaster track has sets of points that allow carriages to transfer from one track to another (for routine maintenance). However, in winter points can freeze and this is extremely dangerous as a carriage can be easily derailed.

The block / systems diagram shows how a heating system works. This warms up points in freezing weather ensuring that they operate safely.

V.Ryan © 2008



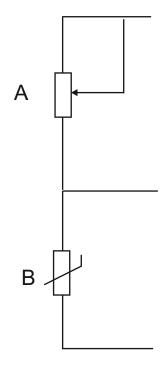The ice sensing part of the circuit is shown below.



Which component acts as a sensor in this circuit?

What does the component sense?

Which component is used to adjust sensitivity of the circuit?


The ice sensing circuit shown above can be altered to sense heat. In the summer the points can expand due to extreme heat. This can also be dangerous. To counter this problem a cooling unit is to be fitted to the points. Complete the next circuit by adding the heat sensor.

## **SYSTEMS DIAGRAM AND TEMPERATURE SENSOR**

WORLD ASSOCIATION OF TECHNOLOGY TEACHERS

https://www.facebook.com/groups/254963448192823/

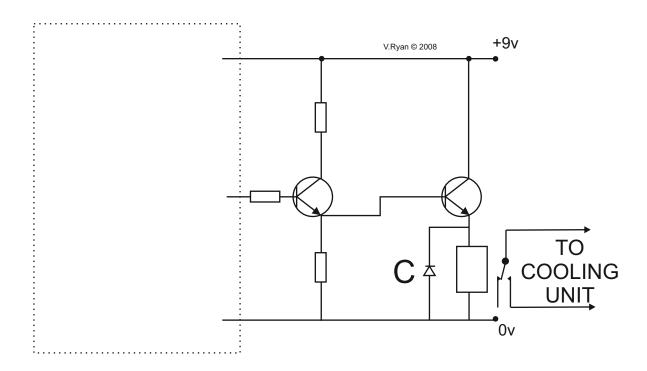www.technologystudent.com © 2017 V.Ryan © 2017



What is the name of component C shown in the heat sensing circuit above?

Name of component C:

What is its function?