

TYPICAL LAYOUT OF A GENIE E18 PIC MICROCONTROLLER PROGRAMMABLE CIRCUIT

DOWNLOAD SOCKET Digital inputs are ... RESET \bigcirc - SWITCH DIGITAL INPUTS E.G._____ • • • • • MICROCONTROLLER INTEGRATED CIRCUIT 5.5 TO 6 VOLT POWER E.G. SOURCE 0 ULN2803 OUTPUTS ରୁନ୍ଦୁ ନୁ ନ୍ମ Q Q OUTPUTS STEPPER MOTOR É.G. INTEGRATED CIRCUIT (OPTIONAL) The outputs can vary. LEDs will OUTPUTS provide lights, a buzzer sound (can be programmed to produce a tune), solar motors are an inexpensive way of creating movement.

Complete the diagram below by adding notes / the missing information.