CAPACITORS

V.Ryan © 2000 - 2008

On behalf of The World Association of Technology Teachers

W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet.

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.

THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.

NOT FOR COMMERCIAL USE.

THIS WORK IS PROTECTED BY COPYRIGHT LAW.

IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN www.technologystudent.com

1. What are the main fun	•	9 World Association of Technology Teach Ole circuits?	ers			
2. Capacitors are often u	sed in combination with	a resistor. What type	e of circuit is	this normally? Und	erline	
the correct answer.						
LIGHT	TIMER	COUNTE	:R	SENSO	R	
+9	3. The circuit and LED.	opposite is compose	ed of a powe	er source, switch, ca	pacito	
CAPACITOR +	3a. What hap	3a. What happens when the switch is closed? Power on.				
POWER	LED					
	3b. What hap off.	pens for a short time	when the s	witch is opened? Po	ower	
0v						
4. In the space below dr	-	epresent capacitors. SYMBOL 2		SYMBOL 3		
5. What are the difference	ces between an ELECT	ROLYTIC and NON-	ELECTROL	YTIC capacitors?		
5. Sketch a typical electrolytic capacitor and a typical non-electrolytic capacitor.		ELECTROLYTIC	1	NON-ELECTROLYT	TIC	