

# DIGITAL LOGIC CIRCUITS

V.Ryan © 2000 - 2009

On behalf of The World Association of Technology Teachers

## W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website ([www.technologystudent.com](http://www.technologystudent.com)) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.  
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.  
NOT FOR COMMERCIAL USE.  
THIS WORK IS PROTECTED BY COPYRIGHT LAW.  
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN [www.technologystudent.com](http://www.technologystudent.com)


# DIGITAL LOGIC EXAMINATION QUESTION

V.Ryan © 2009 World Association of Technology Teachers

An electronics company has developed a baby sitting device which warns parents when their child turns on a lamp next to the bed or when the temperature of the room falls.

Sensor **A** is a temperature sensor which outputs **false (0, low, off)** when the room temperature falls below a set level.

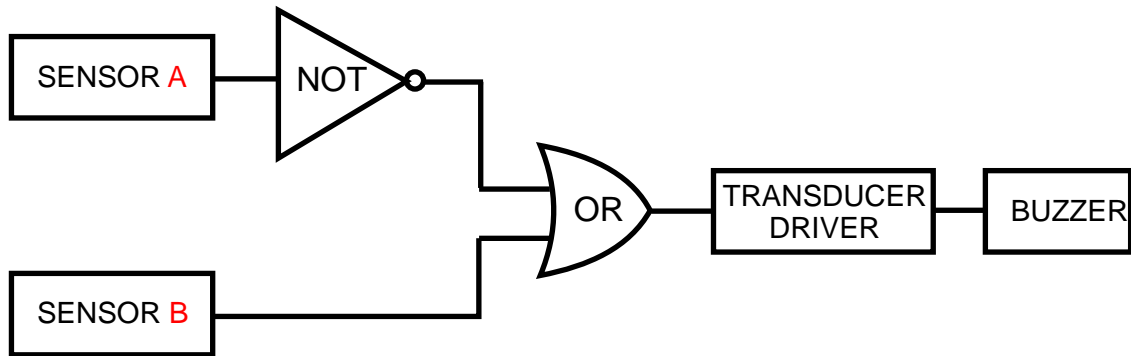
Sensor **B** is a light sensor and is attached to a lamp. The sensor outputs **true (1, high, on)** when the lamp is switched on.



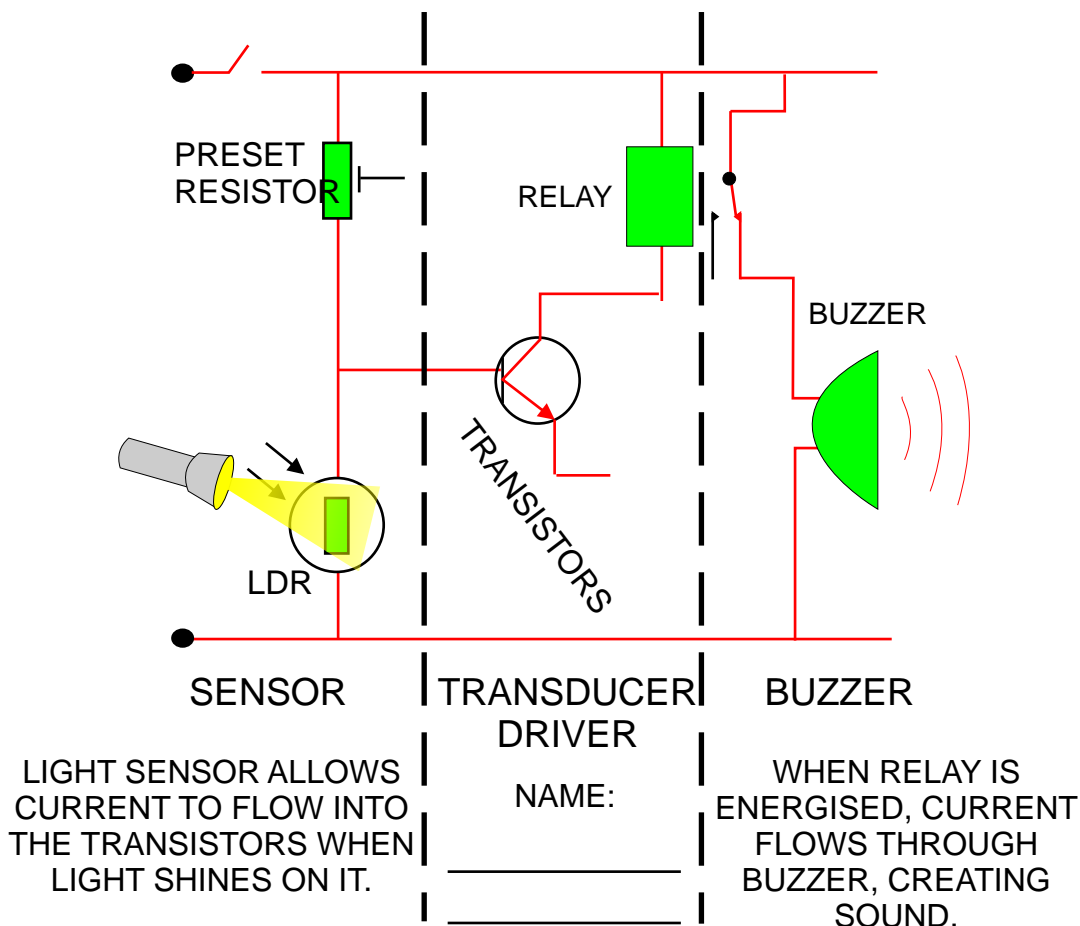**1.** What is a transducer driver and what is its function?

A transducer driver is normally a circuit that amplifies a weak signal (current). In this case current from the OR gate is amplified by the transducer driver which in turn energises a relaying - activating the buzzer. A signal (current) from any gate is usually too weak to directly activate a buzzer.


On the circuit diagram complete the transducer driver and name it.




# DIGITAL LOGIC EXAMINATION QUESTION

V.Ryan © 2009 World Association of Technology Teachers

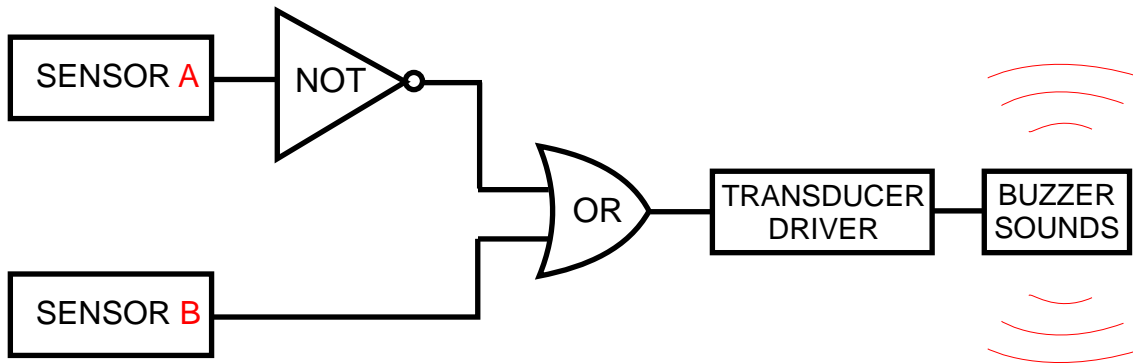2. The young child awakes and turns on a lamp next to her bed, changing the logic states of the outputs / inputs of the sensors and logic gates. On the logic circuit below, write the logic state of inputs / outputs of the sensors and gates.




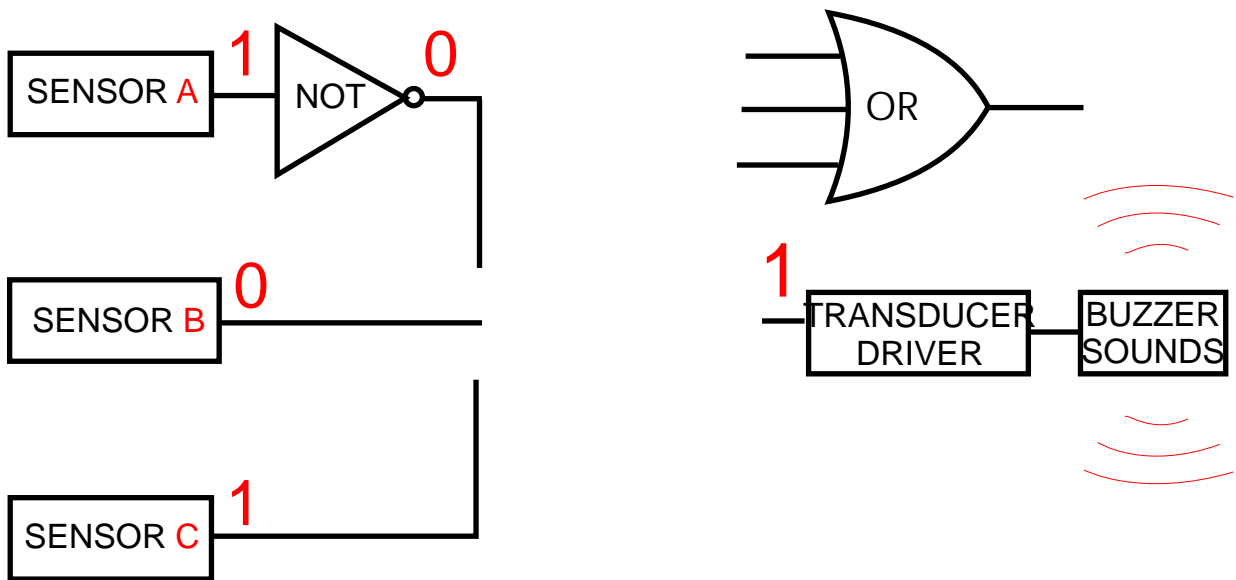3. As the child grows older she regularly gets out of bed and moves around during the night. A new sensor needs to be connected to the system to detect this movement. A micro-switch (SENSOR C) has been added to the system so that when the child opens her bedroom door the buzzer is activated. Complete the circuit below by adding the necessary gate.



### THREE INPUT OR GATE

A	B	C	Q

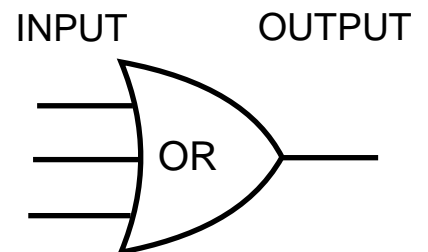

4. In the space opposite write/draw the logic table for your chosen gate.

5. The electronics company has decided to add a circuit that will pulse the buzzer on and off. Name a circuit that could be used.

\_\_\_\_\_