## DUAL TRANSISTOR MULTIVIBRATOR CIRCUIT

V.Ryan © 2000 - 2009

On behalf of The World Association of Technology Teachers

## W.A.T.T.



World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet.

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS. THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS. NOT FOR COMMERCIAL USE. THIS WORK IS PROTECTED BY COPYRIGHT LAW. IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN <u>www.technologystudent.com</u>

## **DUAL TRANSISTOR MULTIVIBRATOR CIRCUIT**

V.Ryan © 2009 World Association of Technology Teachers

1. Describe the multivibrator circuit seen below emphasising the way it works and the function of the components.



2. What will happen if the value of the two electrolytic capacitors are increased?

3. Are the transistors NPN or PNP?

4. What is the function of the 680R resistors?

5. Describe two practical applications of this type of 'flashing' circuit.

<u>A:</u>

<u>B:</u>