

THE 4017B DECADE COUNTER

V.Ryan © 2000 - 2009

On behalf of The World Association of Technology Teachers

W.A.T.T.




World Association of Technology Teachers

This exercise can be printed and used by teachers and students. It is recommended that you view the website (www.technologystudent.com) before attempting the design sheet .

THESE MATERIALS CAN BE PRINTED AND USED BY TEACHERS AND STUDENTS.
THEY MUST NOT BE EDITED IN ANY WAY OR PLACED ON ANY OTHER MEDIA INCLUDING WEB SITES AND INTRANETS.
NOT FOR COMMERCIAL USE.
THIS WORK IS PROTECTED BY COPYRIGHT LAW.
IT IS ILLEGAL TO DISPLAY THIS WORK ON ANY WEBSITE/MEDIA STORAGE OTHER THAN www.technologystudent.com

 6. Below is a 3D view of the decade counter circuit. Label the components.



7. The high power TIP 31A Transistor Circuit can be included as an alternative output to drive motors and solenoids. Describe how this could be used in a project.

